

Scilab Textbook Companion for
Electronic Circuits
by M. H. Tooley¹

Created by
Karan Bhargava
b.tech
Electronics Engineering
Uttarakhand Technical University
College Teacher
Vatsalya Sharma
Cross-Checked by
Ganesh R

August 10, 2013

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Electronic Circuits

Author: M. H. Tooley

Publisher: Elsevier, New Delhi

Edition: 3

Year: 2008

ISBN: 978-81-312-0650-8

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

| | |
|-----------------------------------|----|
| List of Scilab Codes | 4 |
| 1 Electrical Fundamentals | 9 |
| 2 Passive Components | 19 |
| 3 DC Circuits | 32 |
| 4 Alternating voltage and current | 40 |
| 5 Semiconductors | 48 |
| 6 Power Supplies | 52 |
| 7 Amplifiers | 55 |
| 8 Operational Amplifiers | 60 |
| 9 Oscillators | 63 |
| 12 The 555 timer | 65 |
| 13 Radio | 67 |

List of Scilab Codes

| | | |
|----------|--|----|
| Exa 1.4 | Express angle of 215 degree in radians | 9 |
| Exa 1.5 | Express angle in degrees | 9 |
| Exa 1.6 | Calculate the current in milliamp | 10 |
| Exa 1.7 | Express the freq in Mhz of 1495 kHz radio transmitter | 10 |
| Exa 1.8 | Express the capacitance in microfarad of 27000 pF . . | 10 |
| Exa 1.9 | Express current in amp | 11 |
| Exa 1.10 | Express the voltage in millivolt using exp notation . . | 11 |
| Exa 1.11 | Calculate the voltage dropped across 33kohm with 3mA current | 11 |
| Exa 1.12 | Calculate the charge transferred in 20ms by 45 microamp current | 12 |
| Exa 1.13 | Calculate the current supplied to the circuit when 1500V is applied dissipating 300 mW | 12 |
| Exa 1.14 | Calculate the current through resistor 12ohm with 6V battery | 12 |
| Exa 1.15 | Calculate the voltage developed across 56ohm with 100mA current | 13 |
| Exa 1.16 | Calculate the resistance with 15 volt applied with 1mA current | 13 |
| Exa 1.17 | Calculate the resistance of 8m length cooper wire . . . | 14 |
| Exa 1.18 | Calculate the voltage drop between the ends of the 20m wire carring 5A current | 14 |
| Exa 1.19 | Calculate the power supplied by 3 V battery | 14 |
| Exa 1.20 | Calculate the power dissipated in 100ohm with 4V drop | 15 |
| Exa 1.21 | Calculate the power dissipated in 100ohm with 4V drop | 15 |
| Exa 1.22 | Calculate the electric field strength if 2 parallel plates seperated by 25mm are fed by 600V supply | 16 |

| | | |
|----------|--|----|
| Exa 1.23 | Calculate the flux density at 50mm from st wire carrying 20A | 16 |
| Exa 1.24 | Calculate the total flux by flux density | 16 |
| Exa 1.25 | Calculate the relative permittivity of steel at different given flux density | 17 |
| Exa 1.26 | Calculate the current to establish given flux | 17 |
| Exa 2.1 | Determine the tolerance of resistor | 19 |
| Exa 2.2 | Nominal current taken from supply and Max and Min value of supply current | 19 |
| Exa 2.3 | Determine value and type of resistor used for 100mA | 20 |
| Exa 2.4 | Determine the value and tolerance of resistor of brown black red silver | 20 |
| Exa 2.5 | Determine the value and tolerance of resistor of red violet orange gold | 21 |
| Exa 2.6 | Determine the value and tolerance of resistor of green blue black gold | 21 |
| Exa 2.7 | Determine the value and tolerance of resistor of red green black brown | 21 |
| Exa 2.8 | Determine the bands coressponding to 2pt kohm of tolerance 2 percent | 22 |
| Exa 2.9 | Determine the bands coressponding to 4R7K | 22 |
| Exa 2.10 | Determine the bands coressponding to 330RG | 22 |
| Exa 2.11 | Determine the bands coressponding to R22M | 23 |
| Exa 2.12 | Determine the effective resistance in Series and Parallel | 23 |
| Exa 2.13 | Determine the effective resistance of the circuit | 23 |
| Exa 2.14 | Determine the resistance required to realize 50 ohm at 2W | 24 |
| Exa 2.15 | Determine the resistance at 80 degree | 24 |
| Exa 2.16 | Determine the resistance at 90 degree | 25 |
| Exa 2.17 | Determine the resistor temperature coeff | 25 |
| Exa 2.18 | Determine the current flow | 25 |
| Exa 2.19 | Determine the charged stored | 26 |
| Exa 2.20 | Determine the potential diff that be applied to 47 uF-capacitor | 26 |
| Exa 2.21 | Determine the required plate area for 1 nF capacitor | 27 |
| Exa 2.22 | Determine the value of capacitance | 27 |
| Exa 2.23 | Determine the value of capacitor 103K | 27 |

| | | |
|----------|---|----|
| Exa 2.24 | Determine the value of tubular capacitor with brown green brown red brown | 28 |
| Exa 2.25 | Determine the effective capacitance | 28 |
| Exa 2.26 | Determine the series combination of capacitors and their voltage rating | 29 |
| Exa 2.27 | Determine the voltage induced | 29 |
| Exa 2.28 | Determine the current that be applied to an inductor . | 29 |
| Exa 2.29 | Determine the numbers of turns required | 30 |
| Exa 2.30 | Determine the parallel combination for 5mH inductor rated at 2A | 30 |
| Exa 2.31 | Determine the effective inductance | 31 |
| Exa 3.1 | Determine the value of current flowing between A B and value of I3 | 32 |
| Exa 3.2 | Determine the value of V2 and value of E3 | 32 |
| Exa 3.3 | Determine the voltage and current in circuit | 33 |
| Exa 3.4 | Determine the output when no load and loaded by 10kohm | 33 |
| Exa 3.5 | Determine the value of parallel shunt resistor | 34 |
| Exa 3.6 | Determine the range of resistances that can be measured | 34 |
| Exa 3.7 | Determine the current flow in 100 ohm load | 35 |
| Exa 3.8 | Determine the voltage produced | 35 |
| Exa 3.9 | Determine the voltage produced | 36 |
| Exa 3.10 | Determine the initial charging current and current that flow 50ms and 100ms after connecting supply After what time does capacitor fully charge | 36 |
| Exa 3.11 | Determine the time taken by the capacitor to fall below 10V | 37 |
| Exa 3.12 | Determine the capacitor voltage 1 minute later | 37 |
| Exa 3.13 | Determine the C R values for sq wave of 1kHz | 38 |
| Exa 3.14 | Determine the C R values for sq wave of 1kHz | 38 |
| Exa 3.15 | Determine the current in the inductor after supply first connected | 38 |
| Exa 3.16 | Determine the inductor voltage 20ms after supply first connected | 39 |
| Exa 4.1 | Determine the instantaneous voltage | 40 |
| Exa 4.2 | Determine the time period of 400 Hz waveform | 40 |
| Exa 4.3 | Determine the freq of 40 ms waveform | 41 |
| Exa 4.4 | Determine the peak value of 240V rms | 41 |
| Exa 4.5 | Determine the rms value of 50mA peak to peak | 41 |

| | | |
|----------|--|----|
| Exa 4.6 | Determine the rms current | 42 |
| Exa 4.7 | Determine the reactance of 1 μ F at 100Hz and 10kHz . | 42 |
| Exa 4.8 | Determine the current flow in capacitor | 43 |
| Exa 4.9 | Determine the reactance of 1mH at 100Hz and 10kHz | 43 |
| Exa 4.10 | Determine the reactance of 1mH at 100Hz and 10kHz | 43 |
| Exa 4.11 | Determine the impedance of the circuit and current fro supply | 44 |
| Exa 4.12 | Determine the power factor of choke and currentt from supply | 44 |
| Exa 4.13 | Determine the value of capacitance required | 45 |
| Exa 4.14 | Determine the current supplied and voltage developed across 100 ohm | 45 |
| Exa 4.15 | Determine the value of secondry voltage | 46 |
| Exa 4.16 | Determine the number of secondary turns and primary current | 46 |
| Exa 5.1 | Determine the resistance of diode when forward current is given and when forward voltage is given | 48 |
| Exa 5.2 | Determine the series resistor required | 48 |
| Exa 5.3 | Determine the Ie emitter current and hfe | 49 |
| Exa 5.4 | Determine the Ie emitter current and hfe | 49 |
| Exa 5.5 | Determine the Ib base current and hfe | 50 |
| Exa 5.6 | Determine the hfe required and collector power dissipa- tion | 50 |
| Exa 5.7 | Determine the I base current and change in collector current | 51 |
| Exa 5.8 | Determine the change in drain current | 51 |
| Exa 6.1 | Determine the peak voltage that appear across load . | 52 |
| Exa 6.2 | Determine the amt of ripple at output | 52 |
| Exa 6.3 | Determine the amt of ripple at output | 53 |
| Exa 6.4 | Determine the series resistor for operation in conjunc- tion with 9V | 53 |
| Exa 6.5 | Determine equiv output resistance and regulation of power supply | 54 |
| Exa 7.1 | Determine voltage gain and current gain and power gain | 55 |
| Exa 7.2 | Determine voltage gain and upper and lower cutoff freq | 55 |
| Exa 7.3 | Determine overall voltage gain with negative feedback | 56 |
| Exa 7.4 | Determine percentage increase in overall voltage gain . | 56 |
| Exa 7.5 | Determine amount of feedback required | 57 |

| | | |
|----------|--|----|
| Exa 7.6 | Determine output voltage produced by input signal of 10mV | 57 |
| Exa 7.7 | Determine of load resistance required | 57 |
| Exa 7.8 | Determine static value of current gain and voltage gain | 58 |
| Exa 7.9 | Determine quiescent value of collector current and voltage and peak to peak output voltage | 58 |
| Exa 8.1 | Determine the value of open loop voltage gain | 60 |
| Exa 8.2 | Determine the value of input current | 60 |
| Exa 8.3 | Determine the slew rate of device | 61 |
| Exa 8.4 | Determine the time taken to change level | 61 |
| Exa 8.6 | Determine the circuit parameters using opamps | 61 |
| Exa 9.1 | Determine the freq of oscillation | 63 |
| Exa 9.2 | Determine the output freq | 63 |
| Exa 9.3 | Determine the value of R3 and R4 | 64 |
| Exa 12.1 | Determine the parameters of timer circuit | 65 |
| Exa 12.2 | Determine the parameters of timer circuit that produce 5V | 65 |
| Exa 12.3 | Design of pulse generator | 66 |
| Exa 12.4 | Design of 5V square wave generator | 66 |
| Exa 13.1 | Determine the frequency of radio signal of wavelength 15m | 67 |
| Exa 13.2 | Determine the frequency of radio signal of 150MHz | 67 |
| Exa 13.3 | Determine the velocity of propagation of radio signal of 30MHz and 8m wavelength | 68 |
| Exa 13.4 | Determine the two possible BFO freq | 68 |
| Exa 13.5 | Determine the range the local oscillator be tuned | 68 |
| Exa 13.6 | Determine the range the local oscillator be tuned | 69 |
| Exa 13.7 | Determine the radiated power | 69 |
| Exa 13.8 | Determine the power and radiation efficiency | 70 |

Chapter 1

Electrical Fundamentals

Scilab code Exa 1.4 Express angle of 215 degree in radians

```
1 //Exa:1.4
2 clc;
3 clear;
4 close;
5 ang_d=215; //given
6 ang_r=ang_d*%pi/180;
7 printf("%f degree angle is %f radians",ang_d,ang_r);
```

Scilab code Exa 1.5 Express angle in degrees

```
1 //Exa:1.5
2 clc;
3 clear;
4 close;
5 ang_r=2.5; //given
6 ang_d=2.5*180/%pi; //angle in degrees
7 printf("%f radians angle is %f degrees",ang_r,ang_d)
  ;
```

Scilab code Exa 1.6 Calculate the current in milliamp

```
1 //Exa:1.6
2 clc;
3 clear;
4 close;
5 i_amp=0.075; //given
6 i_milamp=i_amp*1000; //current in milliamp.
7 printf("%f amp current is %f mA",i_amp,i_milamp);
```

Scilab code Exa 1.7 Express the freq in Mhz of 1495 kHz radio transmitter

```
1 //Exa:1.7
2 clc;
3 clear;
4 close;
5 fq_khz=1495; //given
6 fq_Mhz=fq_khz/1000;
7 printf("%f kHz frequency is %f MHz",fq_khz,fq_Mhz);
```

Scilab code Exa 1.8 Express the capacitance in microfarad of 27000 pF

```
1 //Exa:1.8
2 clc;
3 clear;
4 close;
5 c_pF=27000; //given
6 c_uF=c_pF/1000;
7 printf("%f picofarad capacitance is %f microfarad",
        c_pF,c_uF);
```

Scilab code Exa 1.9 Express current in amp

```
1 //Exa:1.9
2 clc;
3 clear;
4 close;
5 c_mA=7.25; //given
6 c_A=c_mA*1000;
7 printf("%f milliamperere current is %f ampere",c_mA,
        c_A);
```

Scilab code Exa 1.10 Express the voltage in millivolt using exp notation

```
1 //Exa:1.10
2 clc;
3 clear;
4 close;
5 vg_v=3.75*10^-6; //given
6 vg_mv=vg_v*1000;
7 printf("%f volt voltage is %e mV",vg_v,vg_mv);
```

Scilab code Exa 1.11 Calculate the voltage dropped across 33kohm with 3mA current

```
1 //Ex:1.11
2 clc;
3 clear;
4 close;
5 r=33000; //in ohms
```

```
6 i=0.003; //in amp
7 v=i*r;
8 printf("Voltage dropped = %d volts",v);
```

Scilab code Exa 1.12 Calculate the charge transferred in 20ms by 45 microamp current

```
1 //Ex:1.12
2 clc;
3 clear;
4 close;
5 t=20*10^-3; //in sec
6 i=45*10^-6; //in amp
7 q=i*t*10^9;
8 printf("Charge transferred = %f nC",q);
```

Scilab code Exa 1.13 Calculate the current supplied to the circuit when 1500V is applied dissipating 300 mW

```
1 //Ex:1.13
2 clc;
3 clear;
4 close;
5 p=0.3; //in watts
6 v=1500; //in volts
7 i=(p/v)*10^6;
8 printf("Current supplied = %d microamp",i);
```

Scilab code Exa 1.14 Calculate the current through resistor 12ohm with 6V battery

```
1 //Ex:1.14
2 clc;
3 clear;
4 close;
5 r=12;//in ohms
6 v=6;//in volts
7 i=(v/r);
8 printf(" Current = %f Amp",i);
```

Scilab code Exa 1.15 Calculate the voltage developed across 56ohm with 100mA current

```
1 //Ex:1.15
2 clc;
3 clear;
4 close;
5 r=56;//in ohms
6 i=0.1;//in amp
7 v=i*r;
8 printf(" Voltage dropped = %f volts",v);
```

Scilab code Exa 1.16 Calculate the resistance with 15 volt applied with 1mA current

```
1 //Ex:1.16
2 clc;
3 clear;
4 close;
5 v=15;//in volts
6 i=0.001;//in amp
7 r=v/i;
8 printf(" Resistance = %d ohms",r);
```

Scilab code Exa 1.17 Calculate the resistance of 8m length cooper wire

```
1 //Ex:1.17
2 clc;
3 clear;
4 close;
5 p=1.724*10^-8; //in ohm-meter
6 l=8; //in meters
7 a=1*10^-6; //in sq. meter
8 r=(p*l)/a;
9 printf(" Resistance = %f ohms",r);
```

Scilab code Exa 1.18 Calculate the voltage drop between the ends of the 20m wire carrying 5A current

```
1 //Ex:1.18
2 clc;
3 clear;
4 close;
5 p=1.724*10^-8; //in ohm-meter
6 l=20; //in meters
7 a=1*10^-6; //in sq. meter
8 i=5; //in amperes
9 r=(p*l)/a;
10 v=i*r;
11 printf(" Voltage dropped = %f volts",v);
```

Scilab code Exa 1.19 Calculate the power supplied by 3 V battery

```
1 //Ex:1.19
2 clc;
3 clear;
4 close;
5 v=3;//in volts
6 i=1.5;//in amperes
7 p=v*i;
8 printf("Power supplied = %f watts",p);
```

Scilab code Exa 1.20 Calculate the power dissipated in 100ohm with 4V drop

```
1 //Ex:1.20
2 clc;
3 clear;
4 close;
5 v=4;//in volts
6 r=100;//in ohms
7 p=(v^2)/r;
8 printf("Power dissipated = %f watts",p);
```

Scilab code Exa 1.21 Calculate the power dissipated in 100ohm with 4V drop

```
1 //Ex:1.21
2 clc;
3 clear;
4 close;
5 i=20*10^-3;//in amps
6 r=1000;//in ohms
7 p=(i^2)*r;
8 printf("Power dissipated = %f watts",p);
```

Scilab code Exa 1.22 Calculate the electric field strength if 2 parallel plates separated by 25mm are fed by 600V supply

```
1 //Ex:1.22
2 clc;
3 clear;
4 close;
5 v=600;//in volts
6 d=25*10^-3;//in meters
7 E=(v)/d;
8 printf("Electric Field Strength = %d kV/m",E/1000);
```

Scilab code Exa 1.23 Calculate the flux density at 50mm from st wire carrying 20A

```
1 //Ex:1.23
2 clc;
3 clear;
4 close;
5 u=4*pi*10^-7;//in H/m
6 i=20;//in amps
7 d=50*10^-3;//in meters
8 B=(u*i)/(2*pi*d);
9 printf("Flux Density = %e Tesla",B);
```

Scilab code Exa 1.24 Calculate the total flux by flux density

```
1 //Ex:1.24
2 clc;
```

```

3 clear;
4 close;
5 B=(2.5*10^-3); //in Tesla
6 a=(20*10^-4); //in sq. meter
7 flux=B*a;
8 printf("Flux = %e webers",flux);

```

Scilab code Exa 1.25 Calculate the relative permittivity of steel at different given flux density

```

1 //Ex:1.25
2 clc;
3 clear;
4 close;
5 B1=0.6; //in Tesla
6 u1=B1/800;
7 u_r1=u1/(4*pi*10^-7);
8 printf("relative permittivity at 0.6T = %f",u_r1);
9 B2=1.6; //in Tesla
10 u2=0.2/4000;
11 u_r2=u2/(4*pi*10^-7);
12 printf("\n relative permittivity at 1.6T = %f",u_r2);

```

Scilab code Exa 1.26 Calculate the current to establish given flux

```

1 //Ex:1.26
2 clc;
3 clear;
4 close;
5 flux=0.8*10^-3;
6 a=(500*10^-6); //in sq. meter
7 l=0.6; //in meter
8 N=800;

```

```
9 B=flux/a;
10 printf("Flux Density = %e Tesla",B);
11 H=3500; //in A/m
12 i=(H*1)/N;
13 printf("\n Current required = %f amp.s",i);
```

Chapter 2

Passive Components

Scilab code Exa 2.1 Determine the tolerance of resistor

```
1 //Ex:2.1
2 clc;
3 clear;
4 close;
5 marked=220;//in ohms
6 measured=207;//in ohms
7 err=marked-measured;
8 tol=(err/marked)*100;
9 printf("Tolerance = %f %%",tol);
```

Scilab code Exa 2.2 Nominal current taken from supply and Max and Min value of supply current

```
1 //Ex:2.2
2 clc;
3 clear;
4 close;
5 r=39;//in ohms
```

```

6 v=9; //in volts
7 i=(v/r); //in Amps
8 printf(" Current = %d mA", i*1000);
9 tol=0.1; //i.e, 10%
10 r_min=r-(tol*r);
11 i_max=v/r_min;
12 r_max=r+(tol*r);
13 i_min=v/r_max;
14 printf("\n Max. Current = %f mA & Min Current= %f mA"
        , i_max*1000, i_min*1000);

```

Scilab code Exa 2.3 Determine value and type of resistor used for 100mA

```

1 //Ex:2.3
2 clc;
3 clear;
4 close;
5 v=28; //in volts
6 i=0.1; //in A
7 r=v/i;
8 p=v*i;
9 printf(" Resistance Value = %f ohms & Power
        dissipated = %f W", r, p);

```

Scilab code Exa 2.4 Determine the value and tolerance of resistor of brown black red silver

```

1 //Ex:2.4
2 clc;
3 clear;
4 close;
5 r=10*(10^2);
6 printf(" Resistor value = %d ohm", r);

```

```
7 printf("\nTolerance = 10 %%");
```

Scilab code Exa 2.5 Determine the value and tolerance of resistor of red violet orange gold

```
1 //Ex:2.5
2 clc;
3 clear;
4 close;
5 r=27*(10^3);
6 printf("Resistor value = %d ohm",r);
7 printf("\nTolerance = 5 %%");
```

Scilab code Exa 2.6 Determine the value and tolerance of resistor of green blue black gold

```
1 //Ex:2.6
2 clc;
3 clear;
4 close;
5 r=56*(10^0);
6 printf("Resistor value = %d ohm",r);
7 printf("\nTolerance = 5 %%");
```

Scilab code Exa 2.7 Determine the value and tolerance of resistor of red green black brown

```
1 //Ex:2.7
2 clc;
3 clear;
```

```
4 close;
5 r=25*(10^0);
6 printf("Resistor value = %d ohm",r);
7 printf("\nTolerance = 20 %%");
```

Scilab code Exa 2.8 Determine the bands coressponding to 2pt kohm of tolerance 2 percent

```
1 //Ex:2.8
2 clc;
3 clear;
4 close;
5 r=22*(10^3);
6 printf("Bands are Red, Red, Red, Red");
```

Scilab code Exa 2.9 Determine the bands coressponding to 4R7K

```
1 //Ex:2.9
2 clc;
3 clear;
4 close;
5 printf("Resistance = 4.7 ohm with 10%% tolerance");
```

Scilab code Exa 2.10 Determine the bands coressponding to 330RG

```
1 //Ex:2.10
2 clc;
3 clear;
4 close;
5 printf("Resistance = 330 ohms with 2%% tolerance");
```

Scilab code Exa 2.11 Determine the bands coressponding to R22M

```
1 //Ex:2.11
2 clc;
3 clear;
4 close;
5 printf("Resistance = 0.22 ohm with 20%% tolerance");
```

Scilab code Exa 2.12 Determine the effective resistance in Series and Parallel

```
1 //Ex:2.12
2 clc;
3 clear;
4 close;
5 r1=22;//in ohms
6 r2=47;//in ohms
7 r3=33;//in ohms
8 r_ser=r1+r2+r3;
9 printf("Effective resistance in series = %d ohms",
    r_ser);
10 r_parel=((1/r1)+(1/r2)+(1/r3))^-1;
11 printf("\n Effective resistance in parallel = %f
    ohms",r_parel);
```

Scilab code Exa 2.13 Determine the effective resistance of the circuit

```
1 //Ex:2.13
2 clc;
```



```

3 clear;
4 close;
5 r1=4.7; //in ohms
6 r2=47; //in ohms
7 r3=12; //in ohms
8 r4=27; //in ohms
9 r5=r3+r4;
10 r_parel=((1/r5)+(1/r2))^-1;
11 r_eff=r_parel+r1;
12 printf("Effective resistance = %d ohms",r_eff);

```

Scilab code Exa 2.14 Determine the resistance required to realize 50 ohm at 2W

```

1 //Ex:2.14
2 clc;
3 clear;
4 close;
5 printf("Two 100 ohm resistor of 1 W");

```

Scilab code Exa 2.15 Determine the resistance at 80 degree

```

1 //Ex:2.15
2 clc;
3 clear;
4 close;
5 temp_coeff=0.001; //in per degree centigrade
6 r_o=1500; //in ohm
7 t=80; //temperature diff.
8 r_t=r_o*(1+(temp_coeff)*t)
9 printf("Resistance at %d degree = %d ohms",t,r_t);

```

Scilab code Exa 2.16 Determine the resistance at 90 degree

```
1 //Ex:2.16
2 clc;
3 clear;
4 close;
5 temp_coeff=0.0005; //in per degree centigrade
6 r_t1=680; //in ohm
7 t1=20; //temperature diff.
8 t2=90;
9 r_o=r_t1/(1+(temp_coeff)*t1);
10 r_t2=r_o*(1+(temp_coeff)*t2);
11 printf("Resistance at %d degree = %f ohms",t2,r_t2);
```

Scilab code Exa 2.17 Determine the resistor temperature coeff

```
1 //Ex:2.17
2 clc;
3 clear;
4 close;
5 r_o=40; //resis at 0 degree
6 r_t=44; //at 100 degree
7 t=100; //temperature diff.
8 temp_coeff=(1/t)*((r_t/r_o)-1);
9 printf("Temperature Coefficient = %f per degree
    centigrade",temp_coeff);
```

Scilab code Exa 2.18 Determine the current flow

```

1 //Ex:2.18
2 clc;
3 clear;
4 close;
5 V_1=50;
6 V_2=10;
7 dV=V_1-V_2;//in volts
8 dt=0.1;//in seconds
9 C=22*10^-6;
10 i=C*(dV/dt)*1000;//in mA
11 printf("Current flow = %f milliAmps",i);

```

Scilab code Exa 2.19 Determine the charged stored

```

1 //Ex:2.19
2 clc;
3 clear;
4 close;
5 C=10*10^-6;
6 V=250;//in volts
7 Q=V*C*1000;//in millicoulomb
8 printf("Charged stored =%f mC",Q);

```

Scilab code Exa 2.20 Determine the potential diff that be applied to 47 uFcapacitor

```

1 //Ex:2.20
2 clc;
3 clear;
4 close;
5 C=47*10^-6;//in farads
6 W=4;//energy in joules
7 V=sqrt(W/(0.5*C));

```

```
8 printf("Voltage tht be applied = %d volts",V);
```

Scilab code Exa 2.21 Determine the required plate area for 1 nF capacitor

```
1 //Ex:2.21
2 clc;
3 clear;
4 close;
5 E_o=8.85*10^-12;
6 E_r=5.4;
7 C=1*10^-9;
8 d=0.1*10^-3;
9 A=(C*d)/(E_o*E_r)*10^4;
10 printf("Required plate area = %f sq. cm",A);
```

Scilab code Exa 2.22 Determine the value of capacitance

```
1 //Ex:2.22
2 clc;
3 clear;
4 close;
5 E_o=8.85*10^-12;
6 E_r=4.5;
7 n=6; //no. of plates
8 d=0.2*10^-3; //in meter
9 A=20*10^-4; //in sq. meter
10 C={(E_o*E_r*(n-1)*A)/d}*10^11;
11 printf("Capacitance = %d pF",C);
```

Scilab code Exa 2.23 Determine the value of capacitor 103K

```
1 //Ex:2.23
2 clc;
3 clear;
4 close;
5 printf("Capacitance = 10000 pF of 10%%");
```

Scilab code Exa 2.24 Determine the value of tubular capacitor with brown green brown red brown

```
1 //Ex:2.24
2 clc;
3 clear;
4 close;
5 printf("Capacitance = 150 pF of 2%% tolerance at 100
        V");
```

Scilab code Exa 2.25 Determine the effective capacitance

```
1 //Ex:2.25
2 clc;
3 clear;
4 close;
5 C1=2; //in nF
6 C2=4; //in nF
7 C3=2;
8 C4=4;
9 C_a=C1+C2;
10 C_b=C_a*C3/(C_a+C3);
11 C_eff=C4+C_b;
12 printf("Capacitance = %f nF",C_eff);
```

Scilab code Exa 2.26 Determine the series combination of capacitors and their voltage rating

```
1 //Ex:2.26
2 clc;
3 clear;
4 close;
5 C=100; //in uF
6 C_eff=C*C/(C+C);
7 printf("Two capacitors of %d uF be in parallel used
  to make %d uF capacitance",C,C_eff);
```

Scilab code Exa 2.27 Determine the voltage induced

```
1 //Ex:2.27
2 clc;
3 clear;
4 close;
5 L=600*10^-3; //in H
6 I1=6; //in A
7 I2=2; //in A
8 dI=I1-I2;
9 dt=250*10^-3; //in sec.
10 E=-L*(dI/dt);
11 printf("Induced voltage = %f volts",E);
```

Scilab code Exa 2.28 Determine the current that be applied to an inductor

```
1 //Ex:2.28
2 clc;
3 clear;
4 close;
```

```

5 E=2.5; //energy in joules
6 L=20*10^-3; //in henry
7 I=sqrt(E/(0.5*L));
8 printf("Current = %f A",I);

```

Scilab code Exa 2.29 Determine the numbers of turns required

```

1 //Ex:2.29
2 clc;
3 clear;
4 close;
5 u_o=12.57*10^-7;
6 u_r=500;
7 A=15*10^-4; //area of cross-section in sq. meters
8 l=20*10^-2; //length
9 L=100*10^-3; //in henry
10 n=sqrt((L*l)/(u_r*u_o*A));
11 printf("Inductor requires %d turns of wire",n);

```

Scilab code Exa 2.30 Determine the parallel combination for 5mH inductor rated at 2A

```

1 //Ex:2.30
2 clc;
3 clear;
4 close;
5 //L=(L1*L2)/(L1+L2)
6 L_eq=5; //in millihenry
7 printf("Inductor of 10 mH wired in parallel would
   provide %d mH",L_eq);

```

Scilab code Exa 2.31 Determine the effective inductance

```
1 //Ex:2.31
2 clc;
3 clear;
4 close;
5 L1=60; //in mH
6 L2=60; //in mH
7 L_a=L1+L2;
8 L3=120; //in mH
9 L_b=L_a*L3/(L_a+L3);
10 L4=50; //in mH
11 L_eq=L4+L_b;
12 printf("Equivalent Inductance = %d mH",L_eq);
```

Chapter 3

DC Circuits

Scilab code Exa 3.1 Determine the value of current flowing between A B and value of I3

```
1 //Ex:3.1
2 clc;
3 clear;
4 close;
5 i1=1.5;
6 i2=2.7; //in amp.s
7 i5=i1+i2;
8 i4=3.3;
9 i3=i4+i5;
10 printf("Current b/w A & B = %f A",i5);
11 printf("\n Current I3 = %f A",i3);
```

Scilab code Exa 3.2 Determine the value of V2 and value of E3

```
1 //Ex:3.2
2 clc;
3 clear;
```

```
4 close;
5 E1=6;
6 E2=3;
7 V2=E1-E2;
8 V1=4.5;
9 E3=V1-E2;
10 printf(" Value of V2 = %f A",V2);
11 printf("\n Value of E3 = %f A",E3);
```

Scilab code Exa 3.3 Determine the voltage and current in circuit

```
1 //Ex:3.3
2 clc;
3 clear;
4 close;
5 V1=7.5;//in volts
6 V2=4.5;
7 V3=4.5;
8 r1=110;//in ohms
9 r2=33;
10 r3=22;
11 i1=V1/r1;
12 i2=V2/r2;
13 i3=V3/r3;
14 printf(" Current I1 = %f A",i1);
15 printf("\n Current I2 = %f A",i2);
16 printf("\n Current I3 = %f A",i3);
```

Scilab code Exa 3.4 Determine the output when no load and loaded by 10kohm

```
1 //Ex:3.4
2 clc;
```

```

3 clear;
4 close;
5 V_in=5; //in volts
6 r1=4000;
7 r2=1000;
8 r_p=r1*r2/(r1+r2);
9 V_out=V_in*(r2/(r1+r2));
10 V_out_p=V_in*(r_p/(r_p+r2));
11 printf("output voltage at no load = %f A",V_out);
12 printf("\n output voltage when loaded by 10kohms =
    %f A",V_out_p);

```

Scilab code Exa 3.5 Determine the value of parallel shunt resistor

```

1 //Ex:3.5
2 clc;
3 clear;
4 close;
5 I_in=5; //in mA
6 R_m=100;
7 I_m=1;
8 R_s=R_m*I_m/(I_in-1);
9 printf("Value of parallel shunt resistor = %d A",R_s
    );

```

Scilab code Exa 3.6 Determine the range of resistances that can be measured

```

1 //Ex:3.6
2 clc;
3 clear;
4 close;
5 r1=100;

```

```

6 r2=1000;
7 R_x_1=(r2/r1)*10000;
8 R_x_2=(r1/r2)*10;
9 printf("Range extends from %d ohms to %d ohms",R_x_2
    ,R_x_1);

```

Scilab code Exa 3.7 Determine the current flow in 100 ohm load

```

1 //Ex:3.7
2 clc;
3 clear;
4 close;
5 E=10;
6 r1=500;
7 r2=600;
8 r3=500;
9 r4=400;
10 V_a=E*(r2/(r1+r2));
11 V_b=E*(r4/(r3+r4));
12 V_oc=V_a-V_b;
13 r=((r1*r2)/(r1+r2))+((r3*r4)/(r3+r4));
14 i=(V_oc/(r+100))*1000;
15 printf("Current flow in 100 ohm resistor = %f mA",i
    );

```

Scilab code Exa 3.8 Determine the voltage produced

```

1 //Ex:3.8
2 clc;
3 clear;
4 close;
5 I_sc=19; //in uA
6 R=1000;

```

```

7 R_m=968;
8 V_out=I_sc*(R*R_m/(R+R_m));
9 printf("Voltage produced = %d uV",V_out);

```

Scilab code Exa 3.9 Determine the voltage produced

```

1 //Ex:3.9
2 clc;
3 clear;
4 close;
5 c=1*10^-6;//in farads
6 r=3.3*10^6;//in ohms
7 t=1;//in sec.
8 V_s=9;//in volts
9 V_c=V_s*(1-%e^(-t/(r*c)));
10 printf("Voltage produced = %f V",V_c);

```

Scilab code Exa 3.10 Determine the initial charging current and current that flow 50ms and 100ms after connecting supply After what time does capacitor fully charge

```

1 //Ex:3.10
2 clc;
3 clear;
4 close;
5 c=100*10^-6;//in farads
6 r=1*10^3;//in ohms
7 t1=50*10^-3;//in sec.
8 t2=100*10^-3;//in sec.
9 V_s=350;//in volts
10 i1=(V_s/1000)*(%e^(-t1/(r*c)));
11 i2=(V_s/1000)*(%e^(-t2/(r*c)));

```

```
12 printf("Charging current after %f sec = %f A",t1,i1)
    ;
13 printf("\n Charging current after %f sec = %f A",t2,
    i2);
```

Scilab code Exa 3.11 Determine the time taken by the capacitor to fall below 10V

```
1 //Ex:3.11
2 clc;
3 clear;
4 close;
5 c=10*10^-6;//in farads
6 r=47*10^3;//in ohms
7 V_s=20;//in volts
8 V_c=10;
9 t=-c*r*log(V_c/V_s);
10 printf("time taken = %f sec.",t);
```

Scilab code Exa 3.12 Determine the capacitor voltage 1 minute later

```
1 //Ex:3.12
2 clc;
3 clear;
4 close;
5 c=150*10^-6;//in farads
6 r=2*10^6;//in ohms
7 V_s=150;//in volts
8 V_c=0.8187*V_s;
9 printf("Capacitor voltage = %f V",V_c);
```

Scilab code Exa 3.13 Determine the C R values for sq wave of 1kHz

```
1 //Ex:3.13
2 clc;
3 clear;
4 close;
5 r=10*10^3;//in ohms
6 t=1*10^-3;
7 c=(0.1*t/r)*10^9;
8 printf(" Capacitor = %d nF",c);
```

Scilab code Exa 3.14 Determine the C R values for sq wave of 1kHz

```
1 //Ex:3.14
2 clc;
3 clear;
4 close;
5 r=10*10^3;//in ohms
6 t=1*10^-3;
7 c=(10*t/r)*10^6;
8 printf(" Capacitor = %d uF",c);
```

Scilab code Exa 3.15 Determine the current in the inductor after supply first connected

```
1 //Ex:3.15
2 clc;
3 clear;
4 close;
5 L=6;//in henry
6 r=24;//in ohms
7 t=0.1;//in sec.
8 V_s=12;//in volts
```

```
9 i=(V_s/r)*(1-%e^(-t*r/L));
10 printf("current = %f A",i);
```

Scilab code Exa 3.16 Determine the inductor voltage 20ms after supply first connected

```
1 //Ex:3.16
2 clc;
3 clear;
4 close;
5 V_s=5;//in volts
6 V_c=0.8647*V_s;
7 printf("Inductor voltage = %f V",V_c);
```

Chapter 4

Alternating voltage and current

Scilab code Exa 4.1 Determine the instantaneous voltage

```
1 //Ex:4.1
2 clc;
3 clear;
4 close;
5 V_m=20; //in volts
6 f=50; //in Hz
7 t1=2.5*10^-3;
8 t2=15*10^-3;
9 V1=V_m*sin(2*%pi*f*t1);
10 V2=V_m*sin(2*%pi*f*t2);
11 printf(" Voltage at 2.5ms = %f V",V1);
12 printf("\n Voltage at 15ms = %f V",V2);
```

Scilab code Exa 4.2 Determine the time period of 400 Hz waveform

```
1 //Ex:4.2
2 clc;
3 clear;
```

```
4 close;
5 f=400; //in Hz
6 T=1/f;
7 printf("Time period of %d Hz waveform = %f sec",f,T)
    ;
```

Scilab code Exa 4.3 Determine the freq of 40 ms waveform

```
1 //Ex:4.3
2 clc;
3 clear;
4 close;
5 T=40*10^-3; //in Hz
6 f=1/T;
7 printf("Frequency of 40 ms waveform = %f Hz",f);
```

Scilab code Exa 4.4 Determine the peak value of 240V rms

```
1 //Ex:4.4
2 clc;
3 clear;
4 close;
5 V_rms=240; //in Volts
6 V_pk=1.414*V_rms;
7 printf("Peak voltage of %d V RMS voltage = %f V",
    V_rms,V_pk);
```

Scilab code Exa 4.5 Determine the rms value of 50mA peak to peak

```
1 //Ex:4.5
```

```

2  clc;
3  clear;
4  close;
5  I_pk=50*10^-3; //in Amps
6  I_rms=0.353*I_pk;
7  printf("RMS current of 50mA peak current = %f A",
        I_rms);

```

Scilab code Exa 4.6 Determine the rms current

```

1  //Ex:4.6
2  clc;
3  clear;
4  close;
5  V=10; //pk-pk voltage
6  r=1000; //ohms
7  I_pk=V/r; //in Amps
8  I_rms=0.353*I_pk*1000; //milliamps
9  printf("RMS current of 10V peak-peak voltage = %f mA
        ", I_rms);

```

Scilab code Exa 4.7 Determine the reactance of 1uF at 100Hz and 10kHz

```

1  //Ex:4.7
2  clc;
3  clear;
4  close;
5  c=1*10^-6;
6  f1=100;
7  f2=10000;
8  X_c1=1/(2*%pi*f1*c);
9  X_c2=1/(2*%pi*f2*c);
10 printf("Reactance at 100Hz = %f mA", X_c1);

```

```
11 printf("\n Reactance at 10kHz = %f mA",X_c2);
```

Scilab code Exa 4.8 Determine the current flow in capacitor

```
1 //Ex:4.8
2 clc;
3 clear;
4 close;
5 V=240;
6 c=100*10^-9;
7 f=50;
8 X_c=1/(2*pi*f*c);
9 I_c=V/X_c;
10 printf("Current flow = %f A",I_c);
```

Scilab code Exa 4.9 Determine the reactance of 1mH at 100Hz and 10kHz

```
1 //Ex:4.9
2 clc;
3 clear;
4 close;
5 L=1*10^-3;
6 f1=100;
7 f2=10000;
8 X_L1=(2*pi*f1*L);
9 X_L2=(2*pi*f2*L);
10 printf("Reactance at 100Hz = %f ohm",X_L1);
11 printf("\nReactance at 10kHz = %f ohm",X_L2);
```

Scilab code Exa 4.10 Determine the reactance of 1mH at 100Hz and 10kHz

```

1 //Ex:4.10
2 clc;
3 clear;
4 close;
5 L=1*10^-3;
6 f1=100;
7 f2=10000;
8 X_L1=(2*%pi*f1*L);
9 X_L2=(2*%pi*f2*L);
10 printf("Reactance at 100Hz = %f ohm",X_L1);
11 printf("\nReactance at 10kHz = %f ohm",X_L2);

```

Scilab code Exa 4.11 Determine the impedance of the circuit and current from supply

```

1 //Ex:4.11
2 clc;
3 clear;
4 close;
5 C=2*10^-6;
6 f=400;
7 V=115;
8 X_C=1/(2*%pi*f*C);
9 r=199;
10 z=sqrt(r^2+X_C^2);
11 I_s=V/z;
12 printf("Reactance = %f ohm",X_C);
13 printf("\n Current = %f A",I_s);

```

Scilab code Exa 4.12 Determine the power factor of choke and current from supply

```

1 //Ex:4.12

```

```

2  clc;
3  clear;
4  close;
5  L=150*10^-3;
6  f=400;
7  V=115;
8  X_L=(2*%pi*f*L);
9  r=250;
10 z=sqrt(r^2+X_L^2);
11 I_s=V/z;
12 printf("Reactance = %f ohm",X_L);
13 printf("\n Current = %f A",I_s)

```

Scilab code Exa 4.13 Determine the value of capacitance required

```

1  //Ex:4.13
2  clc;
3  clear;
4  close;
5  L=100*10^-3;
6  f=400;
7  C=(1/(4*%pi*%pi*f*f*L))*10^6;
8  printf("Capacitance required = %f uF",C);

```

Scilab code Exa 4.14 Determine the current supplied and voltage developed across 100 ohm

```

1  //Ex:4.14
2  clc;
3  clear;
4  close;
5  L=20*10^-3;
6  f=2000;

```

```

7 V=1.5;
8 r=100;
9 C=10*10^-9;
10 X_L=(2*%pi*f*L);
11 X_C=1/(2*%pi*f*C);
12 z=sqrt(r^2+(X_L-X_C)^2);
13 i=V/z;
14 v=i*r;
15 printf("Current supplied = %f mA",i);
16 printf("\nVoltage developed = %f V",v);

```

Scilab code Exa 4.15 Determine the value of secondary voltage

```

1 //Ex:4.15
2 clc;
3 clear;
4 close;
5 N_s=120;
6 V_p=220;
7 N_p=2000;
8 V_s=N_s*V_p/N_p;
9 printf("Secondary voltage = %f V",V_s);

```

Scilab code Exa 4.16 Determine the number of secondary turns and primary current

```

1 //Ex:4.16
2 clc;
3 clear;
4 close;
5 V_p=200;
6 V_s=10;
7 N_p=1200;

```

```
8 N_s=N_p*V_s/V_p;
9 i_s=2.5;
10 i_p=N_s*i_s/N_p;
11 printf("Secondary turns = %d ",N_s);
12 printf("\nprimary current = %f A",i_p);
```

Chapter 5

Semiconductors

Scilab code Exa 5.1 Determine the resistance of diode when forward current is given and when forward voltage is given

```
1 //Ex:5.1
2 clc;
3 clear;
4 close;
5 v1=0.43; //volts
6 i1=2.5*10^-3; //in Amps.
7 v2=0.65; //volts
8 i2=7.4*10^-3; //in Amps.
9 r1=v1/i1;
10 r2=v2/i2;
11 printf("Diode resistance for 2.5A current = %d ohms"
        ,r1);
12 printf("\n Diode resistance for 0.65V = %f ohms",r2)
    ;
```

Scilab code Exa 5.2 Determine the series resistor required

```

1 //Ex:5.2
2 clc;
3 clear;
4 close;
5 i=15*10^-3;
6 R=(21-2.2)/i;
7 v=18.8;//in volts
8 P=i*v*1000;
9 printf("Resistor %d ohms of %d mW",R,P);

```

Scilab code Exa 5.3 Determine the I_e emitter current and h_{fe}

```

1 //Ex:5.3
2 clc;
3 clear;
4 close;
5 I_c=30;//in mA
6 I_b=0.6;
7 I_e=I_c+I_b;
8 hfe=I_c/I_b;
9 printf("Emitter current = %f ohms & hfe = %d",
    I_e,hfe);

```

Scilab code Exa 5.4 Determine the I_e emitter current and h_{fe}

```

1 //Ex:5.4
2 clc;
3 clear;
4 close;
5 I_c=30;//in mA
6 I_b=0.6;
7 I_e=I_c+I_b;
8 hfe=I_c/I_b;

```

```
9 printf("Emitter current = %f ohms    &    hfe = %d",
    I_e,hfe);
```

Scilab code Exa 5.5 Determine the I_b base current and hfe

```
1 //Ex:5.5
2 clc;
3 clear;
4 close;
5 I_e=98; //in mA
6 I_c=97;
7 I_b=I_e-I_c;
8 hfe=I_c/I_b;
9 printf("Emitter current = %d mA    &    hfe = %d",
    I_b,hfe);
```

Scilab code Exa 5.6 Determine the hfe required and collector power dissipation

```
1 //Ex:5.6
2 clc;
3 clear;
4 close;
5 I_c=1.5; //in A
6 I_b=50*10^-3;
7 V_ce=6; //volts
8 hfe=I_c/I_b;
9 P=I_c*V_ce;
10 printf("hfe required = %d",hfe);
11 printf("\n collector power dissipation = %d W",P);
```

Scilab code Exa 5.7 Determine the I base current and change in collector current

```
1 //Ex:5.7
2 clc;
3 clear;
4 close;
5 hfe=200
6 I_c=10*10^-3;
7 dI_b=I_c/hfe;
8 dI_c=hfe*dI_b/100;
9 printf("Base current = %f A ",dI_b);
10 printf("\nChange in collector current = %f mA",dI_c)
    ;
```

Scilab code Exa 5.8 Determine the change in drain current

```
1 //Ex:5.8
2 clc;
3 clear;
4 close;
5 dV_gs=0.025;
6 g_fs=-0.5;
7 dI_d=dV_gs*g_fs;//in mA
8 I_d1=50*10^-3;//in mA
9 I_d2=dI_d+I_d1;
10 printf("Change in drain current = %f A",dI_d);
11 printf("\nNew value of drain current = %f A",I_d2);
```

Chapter 6

Power Supplies

Scilab code Exa 6.1 Determine the peak voltage that appear across load

```
1 //Ex:6.1
2 clc;
3 clear;
4 close;
5 V_p=220;
6 V_s=V_p/44;
7 V_pk=1.414*V_s;//in volts
8 V_l=V_pk-0.6;
9 printf("Peak voltage that appear across load = %f V"
    ,V_l);
```

Scilab code Exa 6.2 Determine the amt of ripple at output

```
1 //Ex:6.2
2 clc;
3 clear;
4 close;
5 X_c=3.18;
```

```

6 R=100;
7 V_rip=1*(X_c/sqrt(R^2+X_c^2));
8 printf("Ripple voltage = %f V",V_rip);

```

Scilab code Exa 6.3 Determine the amt of ripple at output

```

1 //Ex:6.3
2 clc;
3 clear;
4 close;
5 f=50;
6 L=10;
7 X_l=2*%pi*f*L;
8 X_c=3.18;
9 V_rip=1*(X_c/sqrt(X_l^2+X_c^2));
10 printf("Ripple voltage = %f V",V_rip);

```

Scilab code Exa 6.4 Determine the series resistor for operation in conjunction with 9V

```

1 //Ex:6.4
2 clc;
3 clear;
4 close;
5 R_l=400;
6 V_in=9;
7 V_z=5;
8 P_z_max=0.5;
9 R_s_max=R_l*((V_in/V_z)-1);
10 R_s_min=((V_z*V_in)-V_z^2)/P_z_max;
11 printf("Suitable value of resistor = %d ohm",
    (R_s_max+R_s_min)/2);

```

Scilab code Exa 6.5 Determine equiv output resistance and regulation of power supply

```
1 //Ex:6.5
2 clc;
3 clear;
4 close;
5 dI_i=20;
6 dV_o=0.5;
7 dV_o_reg=0.1;
8 dI_o=2;
9 R_out=dV_o/dI_o;
10 Regulation=(dV_o_reg/dI_i)*100;
11 printf(" output resis. = %f ohm",R_out);
12 printf(" \n regulation. = %f %%",Regulation);
```

Chapter 7

Amplifiers

Scilab code Exa 7.1 Determine voltage gain and current gain and power gain

```
1 //Ex:7.1
2 clc;
3 clear;
4 close;
5 I_i=4;
6 V_o=2;
7 V_i=50*10^-3;
8 I_o=200;
9 A_v=V_o/V_i;
10 A_i=I_o/I_i;
11 printf(" Volt gain = %f ",A_v);
12 printf("\n Current gain = %f ",A_i);
13 printf("\n Power gain = %f ",A_i*A_v);
```

Scilab code Exa 7.2 Determine voltage gain and upper and lower cutoff freq


```

1 //Ex:7.2
2 clc;
3 clear;
4 close;
5 A_v_max=35;
6 A_v_cutoff=0.707*A_v_max;
7 printf(" Mid-band Volt gain = %f ",A_v_cutoff);
8 printf("\n upper freq = 590Hz & lower freq = 57Hz");

```

Scilab code Exa 7.3 Determine overall voltage gain with negative feedback

```

1 //Ex:7.3
2 clc;
3 clear;
4 close;
5 A=50;
6 b=0.1;
7 G=A/(1+b*A);
8 printf(" overall Volt gain = %f ",G);

```

Scilab code Exa 7.4 Determine percentage increase in overall voltage gain

```

1 //Ex:7.4
2 clc;
3 clear;
4 close;
5 A=50;
6 A_new=A+0.2*A;
7 b=0.1;
8 G=A_new/(1+b*A_new);
9 dG=8.33-G/8.33;

```

```
10 printf(" percentage change in overall volt gain = %f
    %%",dG);
```

Scilab code Exa 7.5 Determine amount of feedback required

```
1 //Ex:7.5
2 clc;
3 clear;
4 close;
5 A=100;
6 G=20;
7 b=(1/G)-(1/A);
8 printf("amount of feedback required = %f ",b);
```

Scilab code Exa 7.6 Determine output voltage produced by input signal of 10mV

```
1 //Ex:7.6
2 clc;
3 clear;
4 close;
5 h_oe=80*10^-6;
6 R_l=10000;
7 I_f=320*10^-6;
8 I_c=I_f*(1/h_oe)/((1/h_oe)+R_l);
9 V_out=I_c*R_l;
10 printf("Output voltage = %f V",V_out);
```

Scilab code Exa 7.7 Determine of load resistance required

```

1 //Ex:7.7
2 clc;
3 clear;
4 close;
5 b=200;
6 h_ie=1.5*10^3; //in ohms
7 h_fe=150;
8 R_l=b*h_ie/h_fe;
9 printf("Load resistance = %d ohms",R_l);

```

Scilab code Exa 7.8 Determine static value of current gain and voltage gain

```

1 //Ex:7.8
2 clc;
3 clear;
4 close;
5 V=9;
6 V_e=2;
7 R4=1000;
8 V_b=2.6;
9 R2=33*10^3;
10 R1=68000;
11 I_r1=(V-V_b)/R1;
12 R3=2.2*10^3;
13 I_b=15.1*10^-6;
14 I_c=2.0151*10^-3;
15 V_r3=I_c*R3;
16 V_c=V-V_r3;
17 printf("Collector voltage = %f V",V_c);

```

Scilab code Exa 7.9 Determine quiescent value of collector current and voltage and peak to peak output voltage

```
1 //Ex:7.9
2 clc;
3 clear;
4 close;
5 V_pp=14.8-3.3;
6 printf("Collector quiescent voltage = 9.2 V");
7 printf("\nCollector quiescent current = 7.3mA");
8 printf("\nOutput peak-peak voltage = %f V",V_pp);
```

Chapter 8

Operational Amplifiers

Scilab code Exa 8.1 Determine the value of open loop voltage gain

```
1 //Ex:8.1
2 clc;
3 clear;
4 close;
5 V_out=2;
6 V_in=400*10^-6;
7 A_v=V_out/V_in;
8 A_v_dB=ceil (20*(log (A_v)/log (10)));
9 printf("open loop voltage gain = %d dB",A_v_dB);
```

Scilab code Exa 8.2 Determine the value of input current

```
1 //Ex:8.2
2 clc;
3 clear;
4 close;
5 V_in=5*10^-3;
6 R_in=2*10^6;
```

```
7 I_in=V_in/R_in;
8 printf("Input current = %e A",I_in);
```

Scilab code Exa 8.3 Determine the slew rate of device

```
1 //Ex:8.3
2 clc;
3 clear;
4 close;
5 V_out=10;
6 t=4;
7 SR=V_out/t;
8 printf("Slew rate = %f V/us",SR);
```

Scilab code Exa 8.4 Determine the time taken to change level

```
1 //Ex:8.4
2 clc;
3 clear;
4 close;
5 V_out=2;
6 SR=15; //in V/us
7 t=V_out/SR;
8 printf("Time taken = %f us",t);
```

Scilab code Exa 8.6 Determine the circuit parameters using opamps

```
1 //Ex:8.6
2 clc;
3 clear;
```

```
4 close;
5 R_in=10000;
6 f1=250;
7 f2=15000;
8 C_in=0.159/(f1*R_in);
9 C_f=0.159/(f2*R_in);
10 printf(" C_f = %e F" ,C_f);
```

Chapter 9

Oscillators

Scilab code Exa 9.1 Determine the freq of oscillation

```
1 //Ex:9.1
2 clc;
3 clear;
4 close;
5 C=10*10^-9;
6 R=10000;
7 f=(1/(2*%pi*sqrt(6)*C*R));
8 printf("The freq of oscillation = %f Hz",f);
```

Scilab code Exa 9.2 Determine the output freq

```
1 //Ex:9.2
2 clc;
3 clear;
4 close;
5 r1=1000;
6 r2=1000;
7 c=100*10^-9;
```



```
8 f=(1/(2*%pi*c*r1));
9 printf("The freq of oscillation at 1 kohm= %f Hz",f)
  ;
10 R1=6000;
11 R2=6000;
12 F=(1/(2*%pi*c*R1));
13 printf("\nThe freq of oscillation at 6 kohm= %f Hz",
  F);
```

Scilab code Exa 9.3 Determine the value of R3 and R4

```
1 //Ex:9.3
2 clc;
3 clear;
4 close;
5 f=1000;
6 t=1/f;
7 C=10*10^-9;
8 R=t/(1.4*C);
9 printf("R= %d kohm",R/1000);
```

Chapter 12

The 555 timer

Scilab code Exa 12.1 Determine the parameters of timer circuit

```
1 //Ex:12.1
2 clc;
3 clear;
4 close;
5 C=100*10^-9;
6 t_on=10*10^-3;
7 R=(t_on/(1.1*C))/1000;
8 printf("R= %f kohm",R);
```

Scilab code Exa 12.2 Determine the parameters of timer circuit that produce 5V

```
1 //Ex:12.2
2 clc;
3 clear;
4 close;
5 C=100*10^-6;
6 t_on=60;
```

```
7 R=(t_on/(1.1*C))/1000;
8 printf("R= %f kohm",R);
```

Scilab code Exa 12.3 Design of pulse generator

```
1 //Ex:12.3
2 clc;
3 clear;
4 close;
5 //R1=R2=R
6 prf=10;
7 C=1*10^-6;
8 R=0.48/(prf*C);
9 printf("R= %d ohm",R);
```

Scilab code Exa 12.4 Design of 5V square wave generator

```
1 //Ex:12.4
2 clc;
3 clear;
4 close;
5 prf=50;
6 C=100*10^-9;
7 R=0.72/(prf*C); //in ohms
8 printf("R= %d kohm",R/1000);
```

Chapter 13

Radio

Scilab code Exa 13.1 Determine the frequency of radio signal of wavelength 15m

```
1 //Ex:13.1
2 clc;
3 clear;
4 close;
5 c=3*108;
6 wl=15;
7 f=c/wl;
8 printf("The frequency =%d Hz",f);
```

Scilab code Exa 13.2 Determine the frequency of radio signal of 150MHz

```
1 //Ex:13.2
2 clc;
3 clear;
4 close;
5 c=3*108;
6 f=150*106;
```

```
7 wl=c/f;  
8 printf("The wavelength =%d m",wl);
```

Scilab code Exa 13.3 Determine the velocity of propagation of radio signal of 30MHz and 8m wavelength

```
1 //Ex:13.3  
2 clc;  
3 clear;  
4 close;  
5 wl=8;  
6 f=30*10^6;  
7 v=f*wl;  
8 printf("The veocity of propagation =%d m/s",v);
```

Scilab code Exa 13.4 Determine the two possible BFO freq

```
1 //Ex:13.4  
2 clc;  
3 clear;  
4 close;  
5 f_rf=162.5;//in kHz  
6 f_af=1.25;//in kHz  
7 f_bfo_max=f_rf+f_af;  
8 f_bfo_min=f_rf-f_af;  
9 printf("The two possible BFO freq. =%f kHz and %f  
kHz",f_bfo_max,f_bfo_min);
```

Scilab code Exa 13.5 Determine the range the local oscillator be tuned

```

1 //Ex:13.5
2 clc;
3 clear;
4 close;
5 f_rf_1=88;//in MHz
6 f_rf_2=108;//in MHz
7 f_if=10.7;//in MHz
8 f_lo_1=f_rf_1+f_if;
9 f_lo_2=f_rf_2+f_if;
10 printf("The range local oscillator be tuned =%f MHz
    & %f MHz",f_lo_1,f_lo_2);

```

Scilab code Exa 13.6 Determine the range the local oscillator be tuned

```

1 //Ex:13.6
2 clc;
3 clear;
4 close;
5 f_rf_1=88;//in MHz
6 f_rf_2=108;//in MHz
7 f_if=10.7;//in MHz
8 f_lo_1=f_rf_1+f_if;
9 f_lo_2=f_rf_2+f_if;
10 printf("The range local oscillator be tuned =%f MHz
    & %f MHz",f_lo_1,f_lo_2);

```

Scilab code Exa 13.7 Determine the radiated power

```

1 //Ex:13.7
2 clc;
3 clear;
4 close;
5 r=12;//in ohms

```

```
6 i=0.5; //in amps
7 P_r=i*i*r; //in W
8 printf("Power radiated = %d W",P_r);
```

Scilab code Exa 13.8 Determine the power and radiation efficiency

```
1 //Ex:13.8
2 clc;
3 clear;
4 close;
5 r=2; //in ohms
6 i=0.5; //in amps
7 P_r=4; //in W
8 P_loss=i*i*r;
9 P_eff=(P_r/(P_r+P_loss))*100;
10 printf("The power loss = %f W",P_loss);
11 printf("\n The power loss = %f %%",P_eff);
```
