

ELECTRONIC CIRCUITS

FUNDAMENTALS AND APPLICATIONS

QUESTION SET C

Target time: 60 minutes

1. Determine the current supplied by each of the three batteries shown in Figure 1. Also, determine the power dissipated in each of the two resistors.

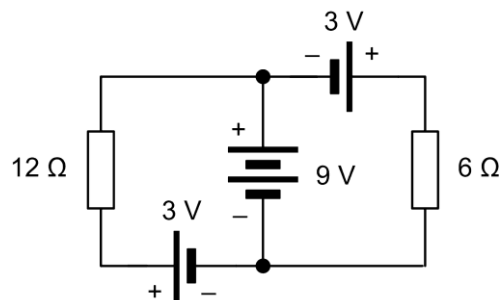


Figure 1 See Question 1

2. Determine the energy stored in a $680 \mu\text{F}$ capacitor when charged from a 400 V DC supply. If the capacitor is subsequently discharged through a $1 \text{ M}\Omega$ resistor, determine the time taken for the capacitor voltage to fall to less than 50 V.

3. A $22 \mu\text{F}$ capacitor is connected to a 12 V, 50 Hz AC supply. Determine the current flowing in the capacitor. Explain why the capacitor doesn't get hot.

4. Part of a repetitive pulse waveform is shown in Figure 2. What is (a) the period; (b) the pulse repetition frequency; (c) the mark-to-space ratio; and (d) the duty cycle of the waveform. Over one complete cycle what will the average voltage of the waveform be?

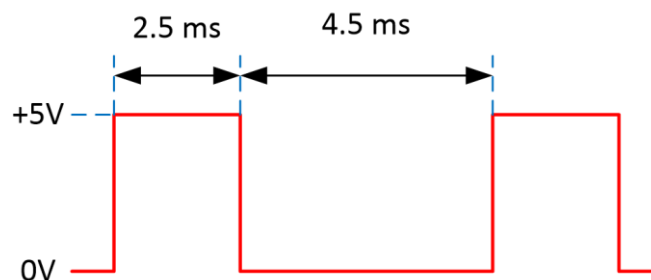


Figure 2 See Question 4

5. Identify the component shown in Figure 3. Sketch the circuit symbol for this component and briefly describe one typical application for it.

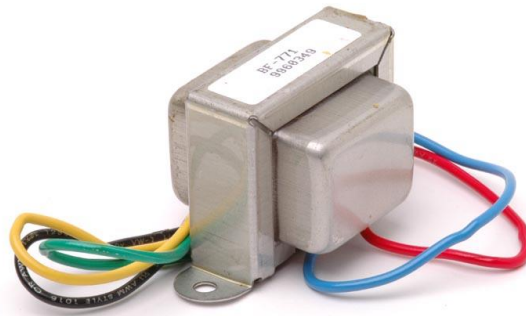


Figure 3 See Question 5

6. A transistor operates with a collector current of 15 mA and a base current of 75 μA . Determine common-emitter current gain and value of collector current that would flow if the base current increases to 100 μA .

7. Identify each of the logic gates shown in Figure 4.

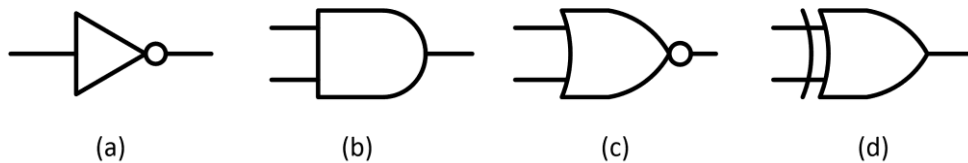


Figure 4 See Question 7

8. Sketch the circuit symbol for an operational amplifier and show how it can be used as a simple fixed-gain inverting amplifier.

9. Sketch the circuit diagram of a monostable timer based on a 555 device. Explain, briefly, how the circuit operates.

10. Convert (a) F6 hexadecimal to binary; (b) 10011010 binary to hexadecimal; (c) 7E hexadecimal to decimal; and (d) 34 decimal to binary.